

Arduino Bootcamp : From Novice to Professional - Learning Through Projects

Controlling an CPU Fan - User Input Control - Part 1

Project Objectives


- In this project you will learn:
 - What is a transistor
 - The different ways a transistor can be used
 - How an npn transistor works
 - Using the Serial Monitor on the Arduino IDE
 - How to accept and process keyboard input in your Arduino programs

Parts

- Arduino Uno
- USB A-B cable
- Breadboard
- CPU Fan
- 220 Ω resistor
- MJE182 npn power transistor
- Connecting wires
- 12V DC Power Supply


What are transistors?

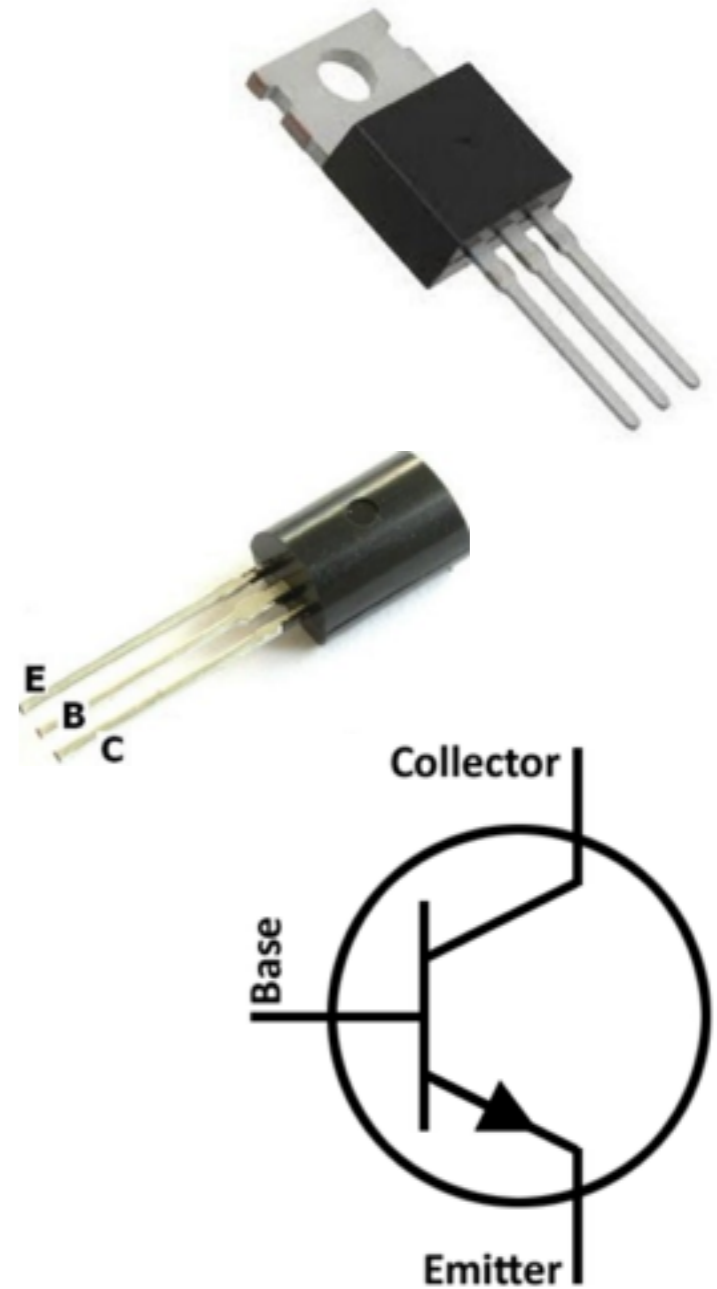- They form the building blocks of the majority of electronic circuitry today
- Semiconductor devices that consist of three leads
 - Base
 - Emitter
 - Collector
- They are essentially miniature electronic switches, which maintain logic state i.e. they have two operating positions – on and off
- Transistors can be connected in circuits to operate as switches or amplifiers




NPN BJT transistor operation

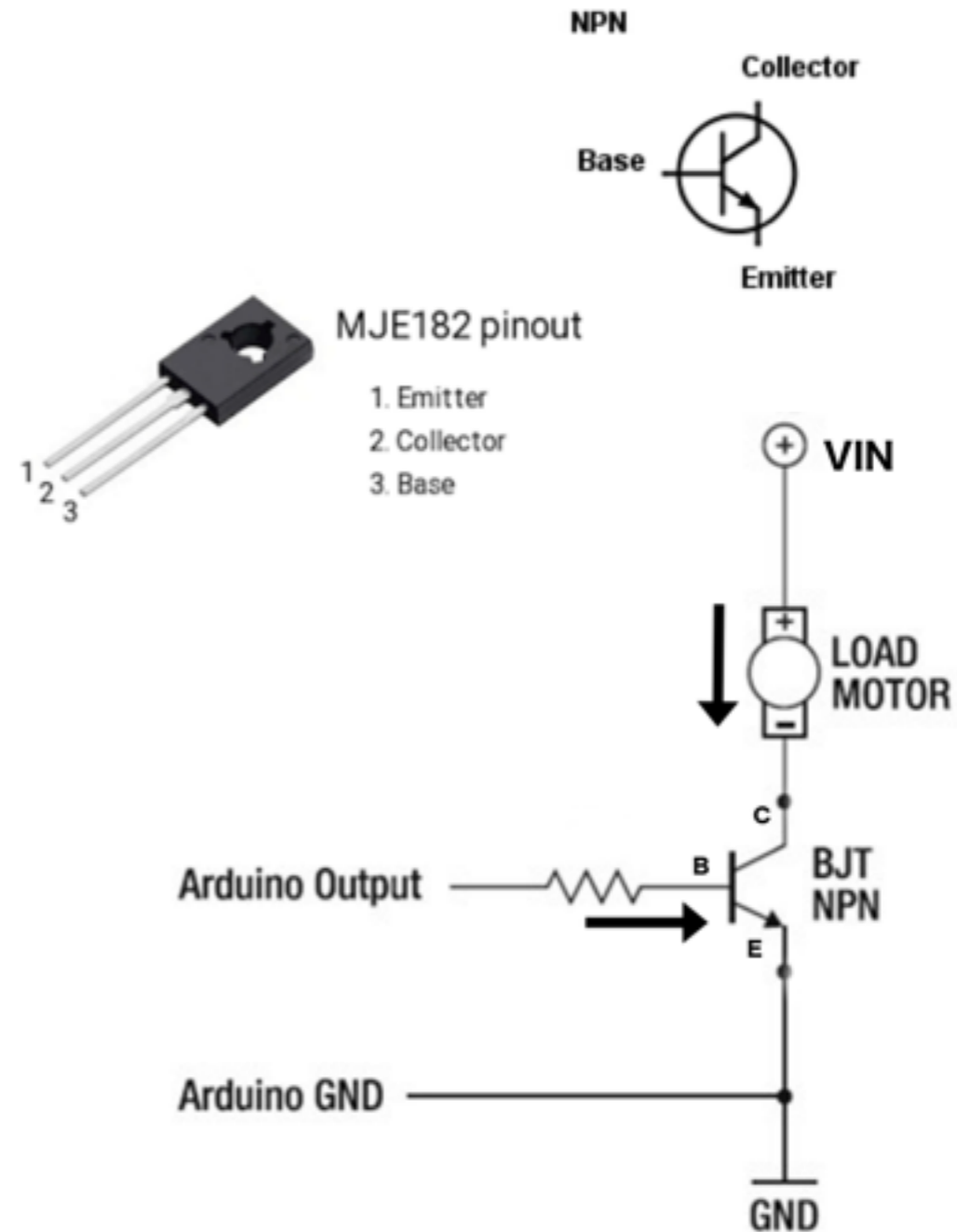- If no base current is flowing, collector current will not flow
- NPN transistor is off and motor is off when there is no base current
- Once base current is applied, collector current flows and the motor will turn on



Circuit Diagram

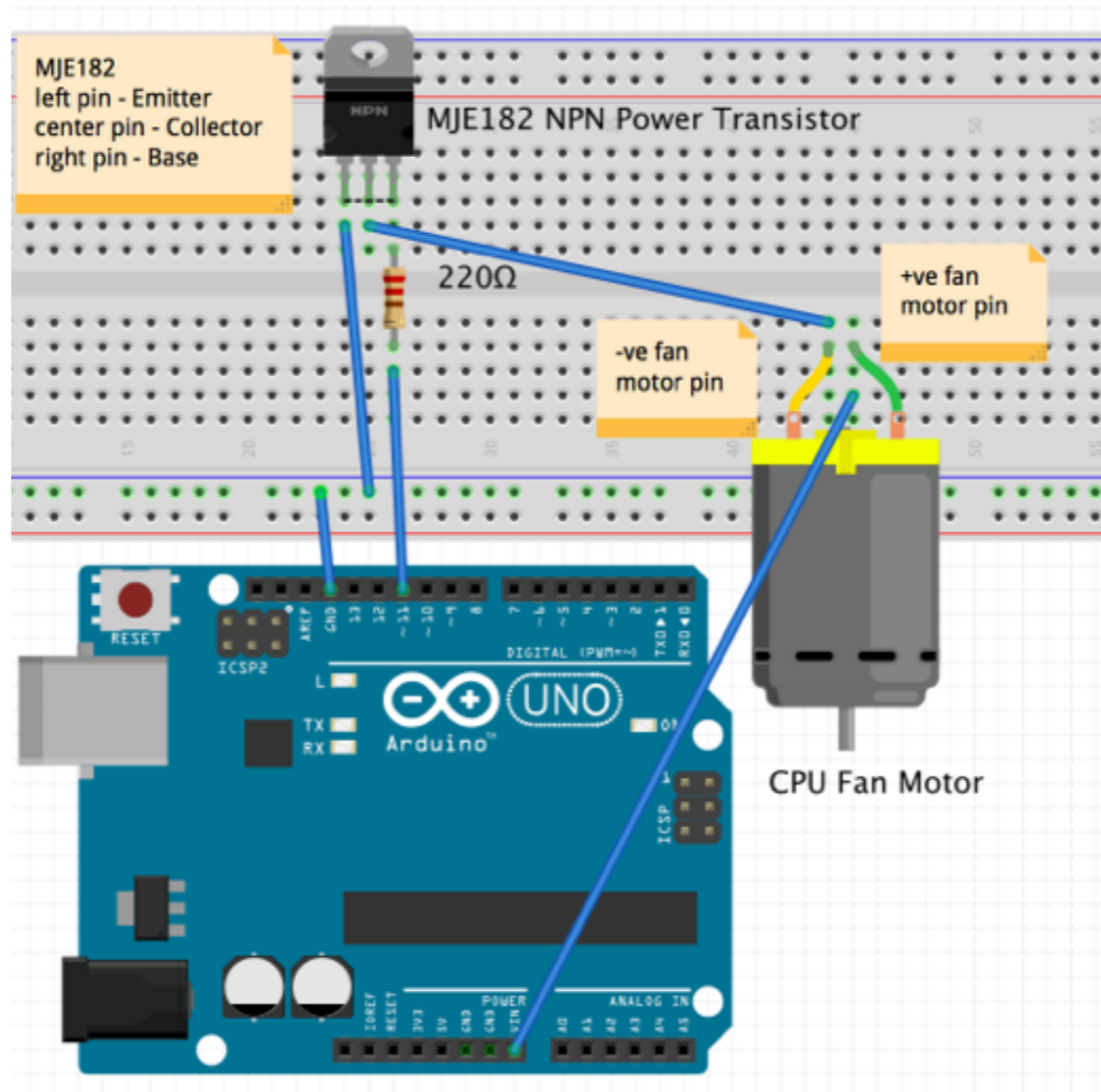

Summary

- In this project you learnt:
 - How a transistor works
 - How to use and connect an npn transistor
 - Using the Serial Monitor in Arduino
 - Accepting and processing keyboard input in your Arduino programs