

# Arduino Bootcamp : Learning Through Projects

Digital Dice

# Project Objectives

- In this project you will learn:
  - How a seven segment display works
  - How to connect a seven segment display in a circuit
  - The difference between a common anode and a common cathode seven segment display

# Parts

- Arduino Uno
- USB A-B cable
- Breadboard
- 7 × 220  $\Omega$  resistors
- 7-Segment Display (Common Cathode)
- Push Button Switch
- Connecting wires

# Seven Segment Displays



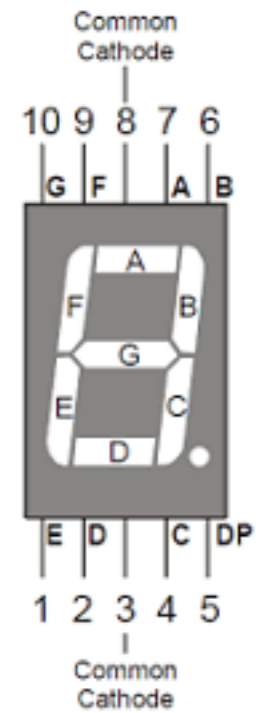
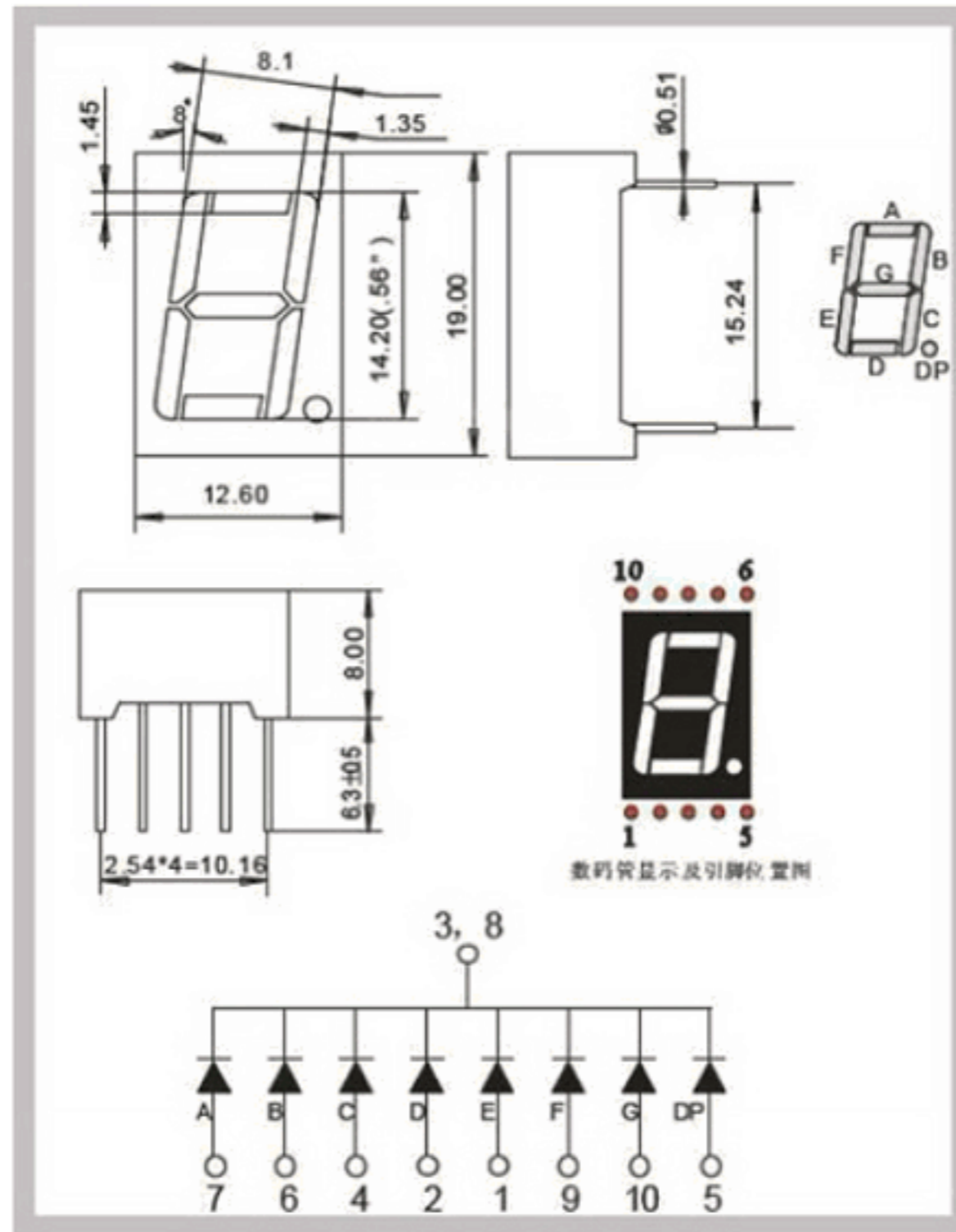
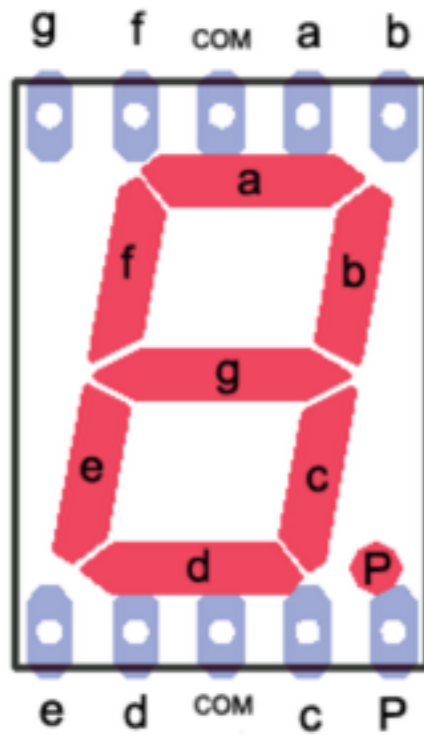


Imagem : Parallax

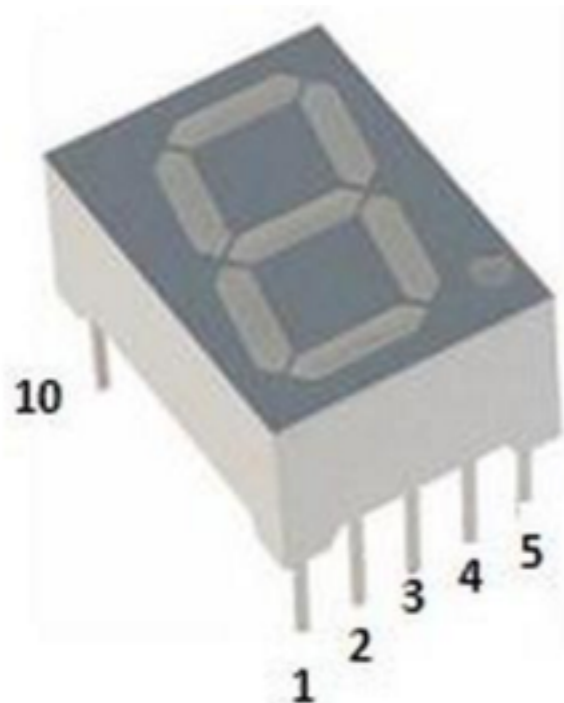


# Common Anode vs Common Cathode


## Common Cathode

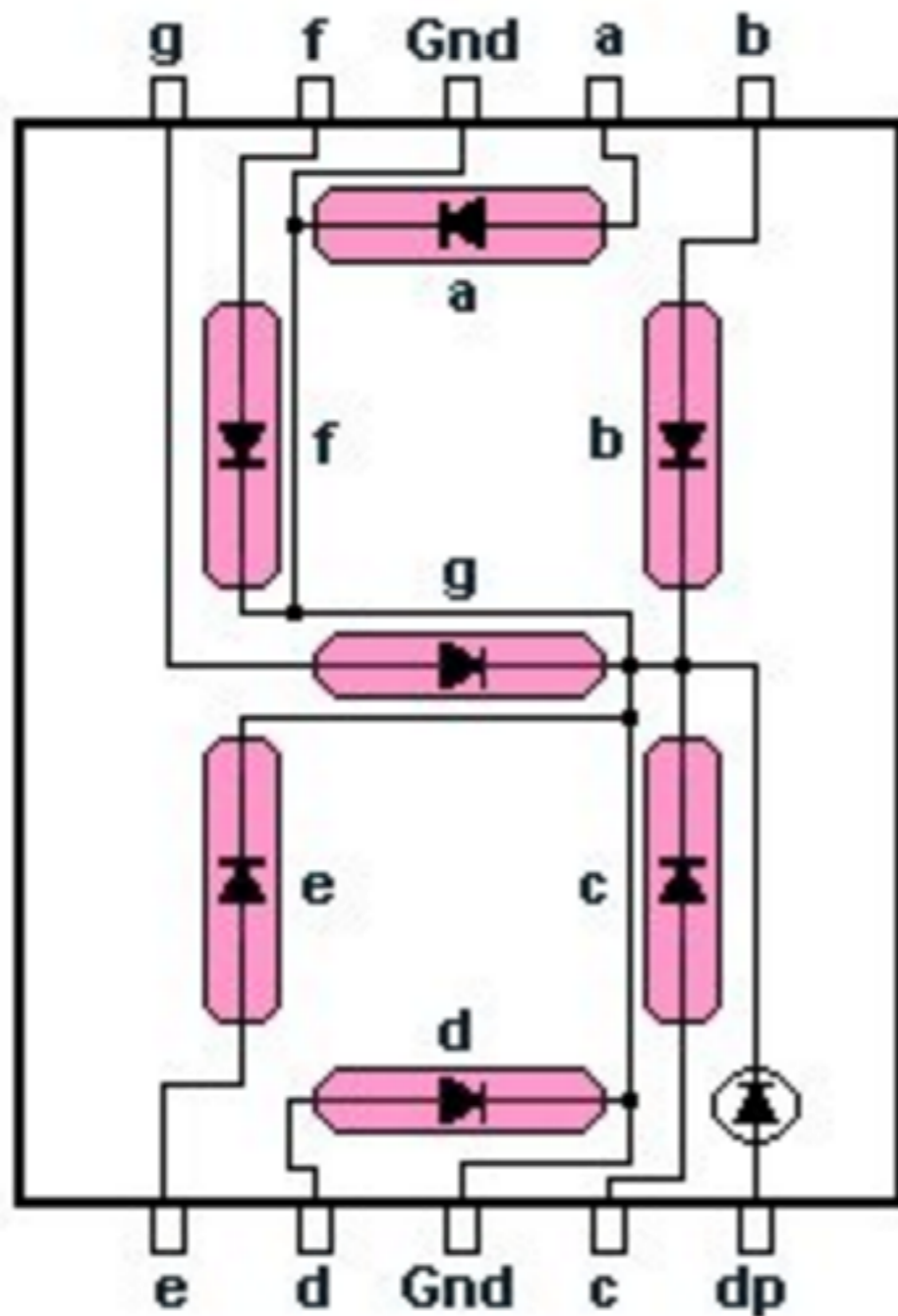


## Common Anode

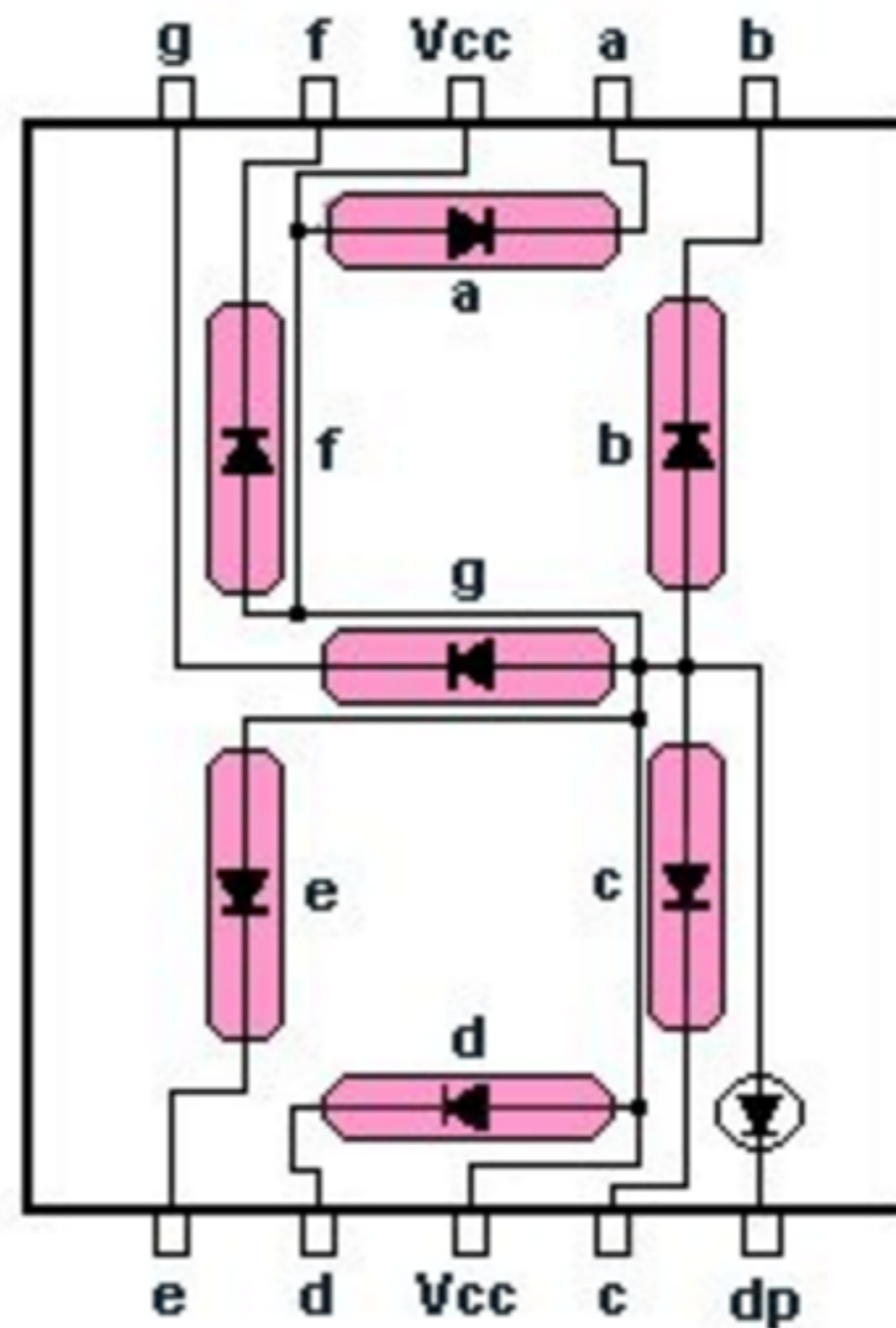

# Circuit Diagram 1

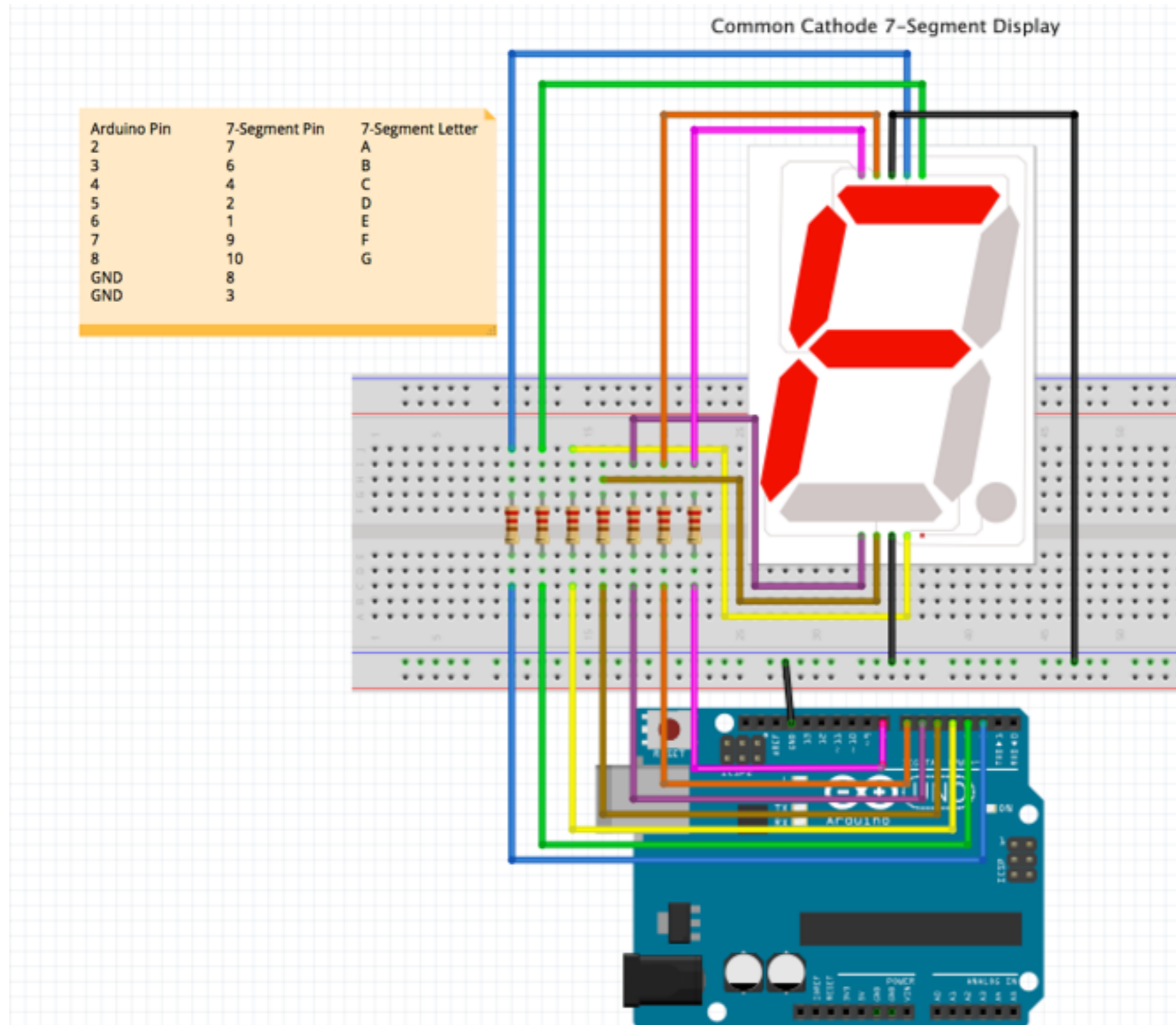

# Circuit Diagram 2

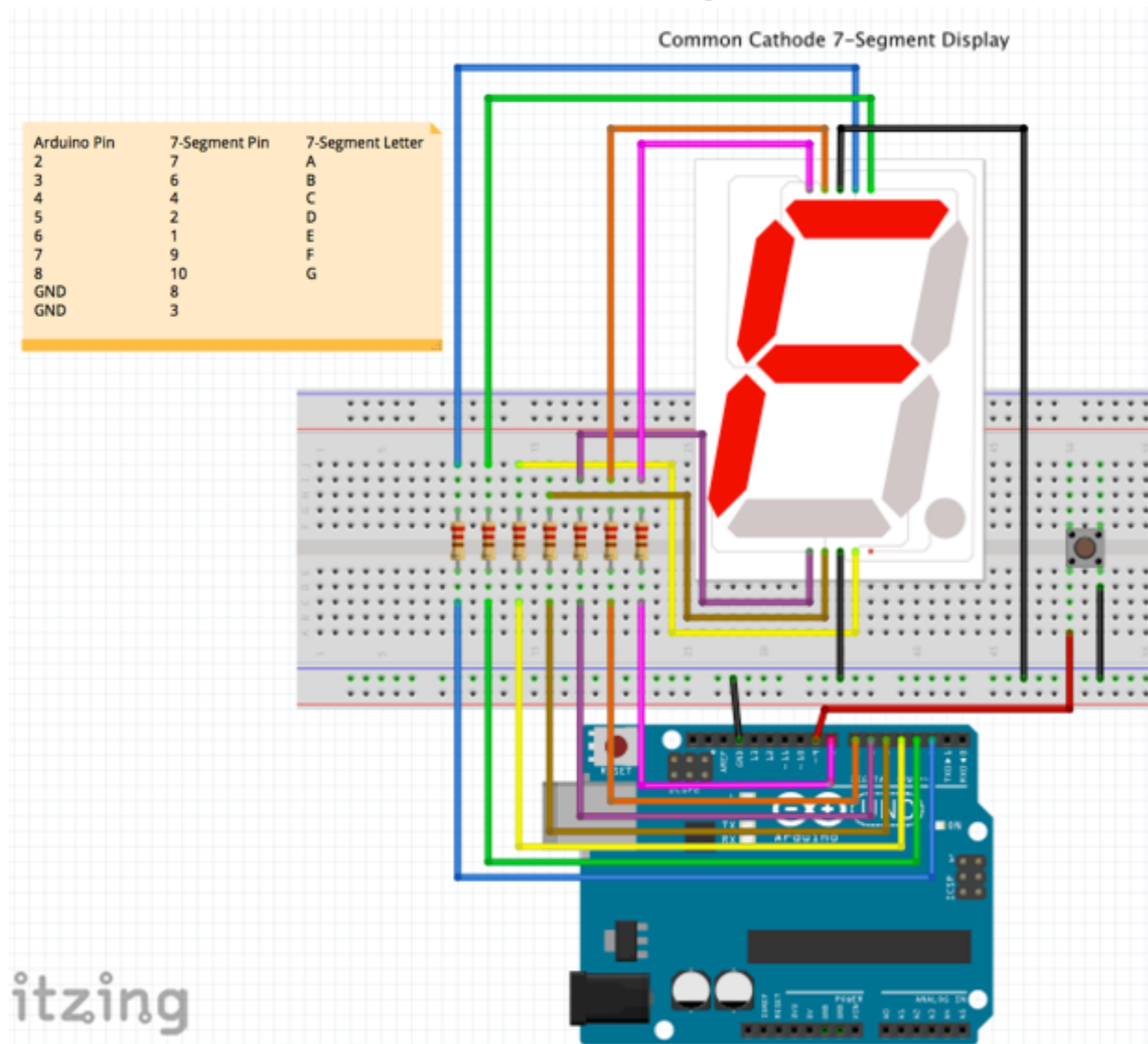

# Summary

- In this project you learnt:
  - What is a seven segment display
  - How to connect a seven segment display in a circuit
  - The difference between common anode and common cathode seven segment displays